

DECA Lab Spring Term

Spring Part 1: EEP1 Datapath & ALU instructions

Department of Electrical and Electronic Engineering

Imperial College London

v1.1

Spring 2024

Contents

1	The EEP1 assembler	1
2	EEP1 ADD & MOV Instructions	2
3	ADDSUB Block design in the ALU	4
4	CMP and AND instructions	4
5	SHIFT instructions	4
6	Reflections	4

Introduction

You are expected to complete Lab1 (this handout) in two weeks.

Before the lab

- Check from the [Issie release page](#) that you have the latest version - if not download it.
- From Spring, Lab1 in the DECA github repository [Download](#) the Lab1-2024 directory.
- Follow Section 1 below to set up the EEP1 assembler on your own laptop, if you have not already done so in class 1
- Check, from Lecture 2, that you understand what each of the inputs and outputs of the `eep1lab1 reg16x8` sheet do, and what type of register file this sheet implements.

In this lab you will learn how ALU instructions work by simulating instruction execution on a nearly complete working EEP1 CPU in issie project `eep1lab1` that implements the EEP1 instruction set described in this Term's lectures. Then, you will analyse the datapath hardware in `lab1` to determine how it works.

`eep1lab1` contains hardware for the EEP1 CPU which is complete except for some of the jump instructions. You will add hardware to implement these in a later lab focusing on the CPU control path. All of this lab can be completed without changing the hardware in `eep1lab1`.

□ **Task 1.** Follow the instructions in the Introduction to download `eep1lab1` Issie project, and update Issie.

1 The EEP1 assembler

The EEP1 assembler tool `eepassembler` converts EEP1 assembly code into machine code. If you have not already done so set up `eepassembler` so that you can convert an assembly code `.txt` file in an Issie project into machine code as follows:

1. [Download](#) and unzip the `eepassembler` software source (or fork and clone the github repo).
2. Put `eepassembler` and `eep1lab1` folders in the same parent folder. Then, for example, the file path to run the assembler on `*.txt` assembly files in the `eep1lab1` directory, as used by the Issie `eep1lab1` project, might be `eepassem ../eep1lab1` (Windows `eepassembler ../eep1lab1`). If you do not follow this you will need to work out the path yourself - or on windows use `chooser.bat` to select the Issie directory.
3. Follow the [README](#) instructions to run the assembler program, and check that it generates four `.ram` files from the four `.txt` files in your `eep1lab1` project.

2 EEP1 ADD & MOV Instructions

You can simulate the EEP1 CPU (`eep1lab1` project) with machine code instructions coming from the `lab1testmovadd.ram` file as follows:

1. Open `lab1testmovadd.ram`, and `lab1testmovadd.txt`. Note that each line of the assembler file generates one 16 bit hex word in the machine code file as specified in Figure 4.
2. Start Issie. Open the `eep1lab1` project you downloaded previously. Open the `eep1` sheet. Select the `Codemem` ROM properties and check the ROM is linked to `lab1testmovadd.ram`. If not change the linking.
3. Check that the `Codemem` ROM has the same data shown in the machine code file by opening up the ROM viewer from properties in Issie.
4. Run the Issie waveform simulator (**Simulations->Wave Simulation** tab). Using the waveform simulator (I) buttons for help if needed, you can adjust the display to make waveforms as in Figure 8. Check that you can do the following:
 - Alter the order of displayed waveforms by dragging.
 - Delete a displayed waveform
 - Add a new displayed waveform by searching for part of its name
 - Change the radix of displayed waveforms
 - Change the position of the cursor by clicking the waveforms.
 - Adjust the grey vertical divider to make the simulation tab larger.
 - Adjust horizontal scale so that you can view the first 8 cycles of the CPU operation while also seeing the value of the PC (PCV) displayed in hex.

□ **Task 2.** Use Issie's waveform simulator to view the first 8 clock cycles of sheet `eep1` simulation using the `lab1testmovadd.txt` instructions. Determine in which clock cycle each instruction executes, and explain the timing and value of waveform changes to the outputs of the register file registers `REGn.Q` on sheet `reg16x8`. For your convenience these outputs are connected to viewers `R0-R7`. Use the instructions in `lab1testmovadd.txt` and the ALU instruction reference in Figure 9.

□ **Task 3.** For both `MOV` and `ADD` instructions with literal and register `op2` (4 cases) choose an example from `lab1testmovadd.txt` and put the instruction into a new four instruction file `lab1test4cases.txt`. Use `eepassembler` to create `lab1test4cases.ram`. Use Figure 4 to calculate the corresponding machine code in binary, then convert it to hexadecimal. Check that your work is in agreement with `lab1test4cases.ram`.

Data flow in the EEP1 datapath for MOV and ADD ALU instructions

Figure 6 shows the top-level schematic sheet of the EEP1 CPU, and Figure 1 the design hierarchy of its `datapath` sheet. Note that you can also see this design hierarchy from the Shee menu of Issie. In this section will work with the EEP1 datapath hardware in the `eep1lab1` project. Specifically, you will trace the logic through the `datapath` and `alu` sheets and work out the required control signals to correctly change a register file register as required by the `MOV` and `ADD` instructions.

Look at the `datapath` sheet (Figure 7). The current instruction word (that is - the machine code for the current instruction) is output from the Instruction ROM and input to `datapath` on its `INS(15:0)` port. Every

 


Figure 1: EEP1 datapath design hierarchy

Block	Select	Use
Datapath.MUX1	AD1SelC	determines REGFILE Port 2 address.
Datapath.MUX2	0	Non-zero for memory load - assume 0 in Lab1.
Datapath.MUX3	0	Non-zero for writing PC to registers (lab2) - assume 0 in Lab1.
ALU.MUX1	OP2Sel	Selects op2 format.
ALU.MUX2	ALUOPC	Selects which ALU operation.
ALU.ADDSUB	n/a	For Section 2 Assume ADDSUB.OUT=ADDSUB.INA+ADDSUB.INB.
EXTEND	n/a	For Lab1 assume EXTEND.IMMEXT = EXTEND.IMMS8 sign extended to 16 bits.
Datapath.REGFILE	n/a	See lecture notes slide 37 for truth table of DOUT as function of AD for each port.

Figure 2: Data flow through datapath block

clock cycle a new instruction will be presented, and the function of the datapath is to change one of the CPU registers contained in REGFILE as specified by this instruction. The instruction word $INS(15:0)$ is interpreted by the **dpdecode** sheet which contains combinational logic that drives control signals in the datapath correctly to implement every instruction.

Figure 7 shows the 16 bit data flow through the datapath from REGFILE. read port(s), through hardware blocks, to the REGFILE write port **Regfile.DIN1**. Figure 2 explains the function of the MUXes and other blocks in this path. The flow of data is controlled by the $INS(15:0)$ instruction word fields **A,B,C,Imm8** that determine which registers (or number) are operands.

Throughout the following sections, when you are asked to write algebraic truth tables, it is expected that you will work these out yourself, one row at a time, rather than use Issie truth tables. You are also expected to use don't cares on row inputs or outputs when operation does not depend on them. For example, the D input of a register is don't care for a row where its enable is 0.

□ **Task 4.** Run the **eep1** sheet of **eep1lab1** with ROM contents from your **lab1test4cases.ram** file. For each of the 4 cases show the values of **Op2Sel**, **AD1SelC** in the waveform simulator. Use this to write a 4 row truth table, one for each instruction, showing the corresponding values of **Op2Sel**, **AD1SelC**.

Analysing the hardware in the **eep1**, **alu** sheets Write a 4 row algebraic truth table showing outputs **REGFILE.DIN1** and **REGFILE.AD1** during the **MOV instruction**, when **ALUOPC=0** is as shown in 4. Your table then has algebraic inputs **A,B,C,Imm8** and binary inputs **Op2Sel**, **AD1SelC**. In your table you can write **REGFILE[a]** to indicate the contents of register number **a** read from **REGFILE**. Write a similar truth table with **ALUOPC** given the its value for **ADD**.

For each instruction in **lab1test4cases.txt**, using the values of **Op2Sel**, **AD1Sel** from your simulation to select the table row, check that the algebraic truth table values of **REGFILE.DIN**, **REGFILE.AD1** implement the register file write specified in Figure 9.

3 ADDSUB Block design in the ALU

Look at the ALU sheet. The ALU.ADDSUB block is responsible for implementing addition and subtraction: its operation depends on the INVERT and ADDSUBBCIN signals which come from the ALU.DECODE block, and via this block are controlled by ALUOPC and FLAGCIN. In this section you will check the logic in the ALU.DECODE block which makes the ALU instructions that require addition or subtraction work.

The 5 instructions ADD, SUB, ADC, SBC, CMP use the ADDSUB block: check this by looking at which ALU.MUX2 inputs are connected to ADDSUB.OUT and noting that MUX2.Se1=ALUOPC. Write an algebraic truth table for ADDSUB.OUT as a function of algebraic inputs INA, INB, CARRYIN and binary input INVERT. Using this, and the specifications in Figure 9 of the 5 instructions, work out a truth table, using don't cares to simplify, for the ALU.DECODE block. This truth table has outputs ALU.DECODE.INVERT, ALU.DECODE.ADDSUBBCIN and inputs ALU.DECODE.ALUOPC, ALU.DECODE.FLAGCIN. For instructions other than the 5 considered here ALU.OUT is don't care. Explain this statement by looking at how ALU.OUT is connected.

□ **Task 5.** Show that the logic given in sheet *aludecode* is compatible with your algebraic truth table. Show that *eep1lab1* is correct for all the instructions in *lab1testarith.txt* by changing instruction ROM sources (Issie properties) and comparing the register values in a simulation with Figure 9.

4 CMP and AND instructions

□ **Task 6.** Look at the logic in the *dpdecode* sheet that drives DP.DECODE.WEN1. Write a truth table that shows the value of WEN1 for each of the 8 ALU instructions. Compare this with Figure 9 to show it is correct. Look at the MUX2 inputs in the *alu* sheet, and the coding of the "AND" instruction, to find what hardware implements it, Check its definition in Issie to make sure it is correct.

□ **Task 7.** Run a simulation of instructions in *lab1testandcmp.txt* and check that all the register value results in this match the instruction definitions in Figure 4.

5 SHIFT instructions

□ **Task 8.** Using the LSL, LSR, ASR, XSR shift instruction definitions from the lectures work out what waveforms you expect from the code in *lab1testshift.txt*. Check this against *eep1lab1* simulation.

These operations are correctly implemented in the *eep1lab1* design by the Shift sheet, which implements all 4 shift instructions, with control inputs SCNT(3:0) and SHIFTOPC(1:0). SCNT controls the number of bits shifted and SHIFTOPC the shift type as specified in Figure 4. The combinational shift logic is implemented by the 4 shift blocks Shift1, Shift2, Shift4, Shift8. Shift n implements SHIFT n .OUT = (SHIFT n .IN shifted by x) where $x = n$ if EN=1, or $x = 0$ (e.g. no shift) if EN=0. The 4 Shift n blocks are connected in series as in shown in *shift*. You may assume that when shift blocks are in series the corresponding shift counts add.

□ **Task 9.** By inspecting the Issie hardware driving SHIFT n .EN, or by noting the values of these signals for different values of SCNT, explain how the correct overall shift is implemented for all values of SCNT.

This design, implementing a variable shift of up to 2^n bits in n stages, is one common implementation of a *barrel shifter* and is often used in CPUs like EEP1 or ARM that implement multi-bit shift instructions.

6 Reflections

In Lab1 you have explored nearly all of the design of the EEP1 datapath, and you will now understand how the CPU ALU instructions are implemented in hardware using a register file and an ALU. Lab2 will focus entirely on the *controlpath* and show how this is implemented, and therefore how the EEP1 decides which address in instruction memory contains the next instruction to be executed. In Lab2 you will complete the EEP1 implementation of the jump instructions, and show how the Flags FlagN, FlagZ, FlagC, FlagV operate.

 


Figure 3: EEP1 ALU sheet

SHIFTOPC(1:0)	Shift
0	LSL
1	LSR
2	ASR
3	XSR

ALUOPC	INS(8)=0	INS(8)=1
0	MOV ¹ Ra, Rb	MOV Ra, #IMM
1	ADD Rc, Ra, Rb	ADD Ra, #IMM
2	SUB Rc, Ra, Rb	SUB Ra, #IMM
3	ADC Rc, Ra, Rb	ADC Ra, #IMM
4	SBC Rc, Ra, Rb	SBC Ra, #IMM
5	AND Rc, Ra, Rb	AND Ra, #IMM
6	CMP ¹ Ra, Rb	CMP Ra, #IMM
7	Shift Ra, Rb, #SCNT (see SHIFTOPC for Shift)	

¹Instruction does not use Rc, this field is (0)

Legend	Meaning
Imm4	4 bit unsigned immediate
Imms8	8 bit signed immediate
(0)	Must be 0 for current instructions, non-zero values are reserved for expansion

EEP1 machine code	INS bit	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
ALU	0	ALUOPC=7				a			Shift-opc(1)	b			Shift-opc(0)	Imm4 (SCNT)			
		ALUOPC=0..6				a			0	b			c		(0)		
									1	Imms8 (IMM)							

Figure 4: EEP1 ALU Instructions and Machine Code

Port	Size	Type	Default	Notes	When
INS	16	Input		Instruction word	This lab
FLAGCIN	1	Input	0	Carry flag input	This lab
FLAGC,FLAGV,FLAGN,FLAGZ	1	Output		Flag control	Lab 2
RAOUT	16	Output		RET instruction	Lab 2
PCIN	16	Input		JSR instruction	Lab 2
MEMDIN, MEMADDR	16	Output		data memory interface	Lab 4
MEMDOUT	16	Input		data memory interface	Lab 4
MEMWEN	1	Output		data memory interface	Lab 4
DPEN	1	Input	1	Enable operation	Lab 5

Figure 5: EEP1 datapath sheet inputs and outputs

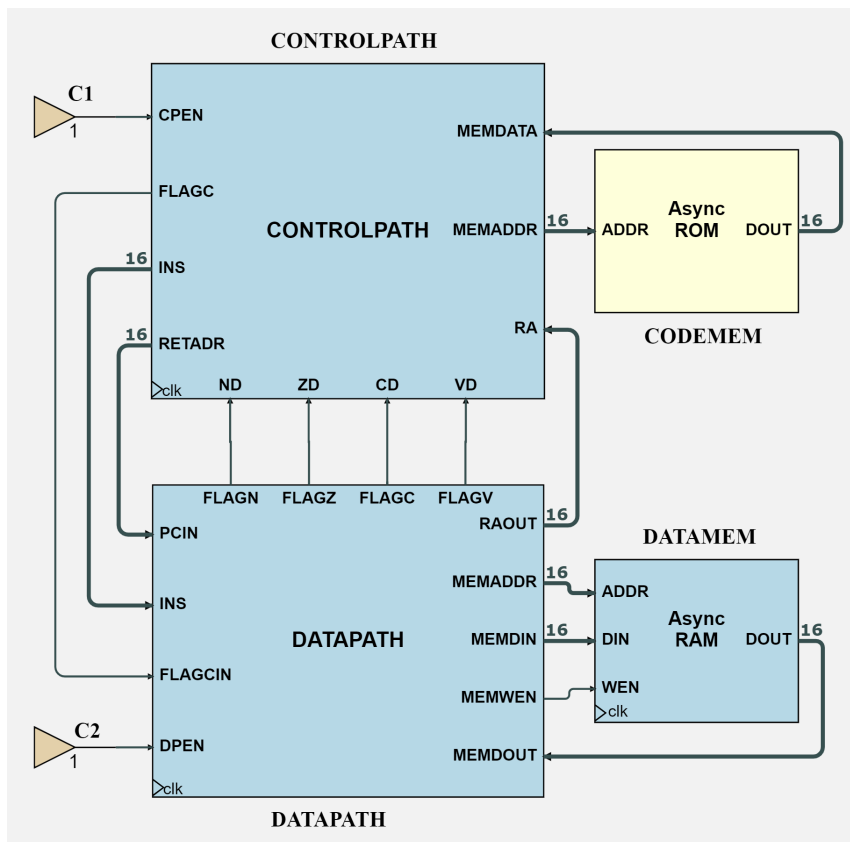


Figure 6: EEP1 CPU

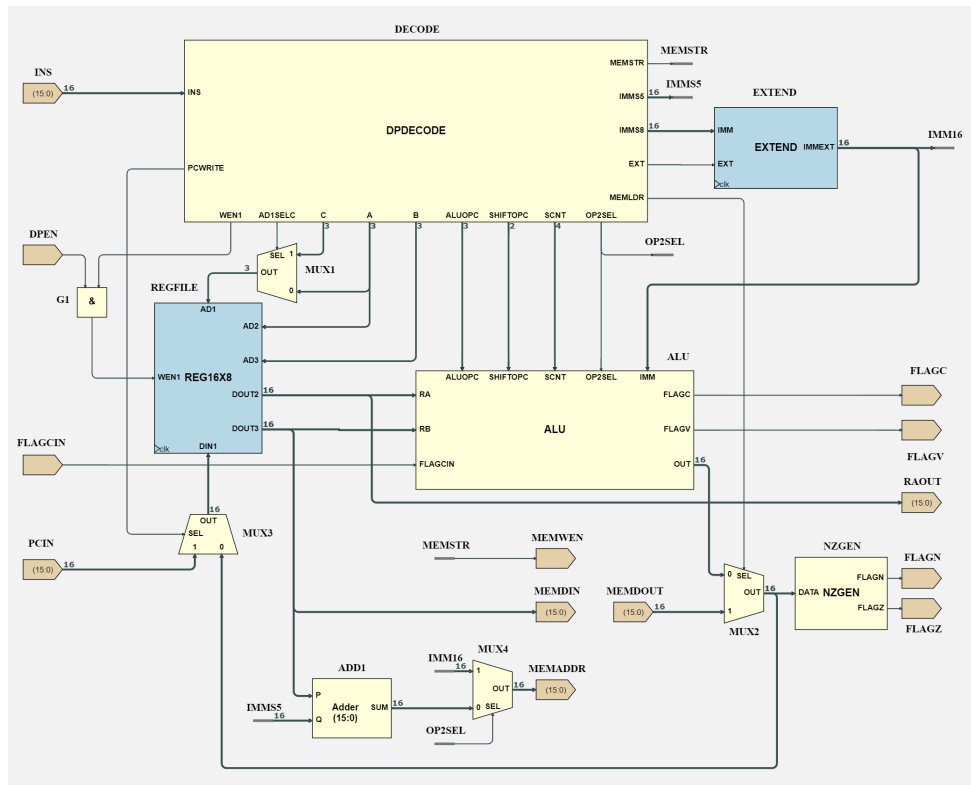


Figure 7: EEP1 Datapath

	0	1	2	3	4	5	6	7	
CONTROLPATH_M.PCV(15:0)	0x0000	0x0001	0x0002	0x0003	0x0004	0x0005	0x0006	0x0007	0x0000
DATAPATH_M.DECODE_M.Ins(15:0)	0x0B03	0x0DFF	0x0F0D	0x00C0	0x1AE4	0x1503	0x19FF		0x0B03
Datapath_m.REG0.Q(15:0)		0x0000	0x0000			0xFFFF		0xFFFF	0x0000
Datapath_m.REG1.Q(15:0)		0x0000	0x0000			0x0010			0x0000
Datapath_m.REG2.Q(15:0)		0x0000	0x0000	0x0000		0x0003			0x0000
Datapath_m.REG3.Q(15:0)		0x0000	0x0000	0x0000	0x0000				0x0000
Datapath_m.REG4.Q(15:0)		0x0000	0x0000	0x0000	0x0000				0x0000
Datapath_m.REG5.Q(15:0)	0x0000		0x0003		0x0003	0x0003		0x0003	0x0000
Datapath_m.REG6.Q(15:0)	0x0000		0xFFFF		0xFFFF	0xFFFF	0xFFFF		0x0000
Datapath_m.REG7.Q(15:0)		0x0000			0x000D	0x000D			0x0000

Figure 8: Simulating EEP1 running lab1testmovadd instructions

EEP1 ALU instructions: detail

OPCALU	Mnemonic	ALU.Out: INS(8)=0	ALU.Out: INS(8) = 1	Write FlagC ¹	Write register	
0	MOV	Rb	Imm	No	Ra	move
1	ADD	Ra + Rb	Ra + Imm	Yes	Rc (Ra if INS(8)=1)	arithmetic
2	SUB	Ra - Rb	Ra - Imm	Yes	Rc (Ra if INS(8)=1)	
3	ADC	Ra + Rb + C	Ra + Imm + C	Yes	Rc (Ra if INS(8)=1)	
4	SBC	Ra - Rb + (C-1)	Ra - Imm + (C-1)	Yes	Rc (Ra if INS(8)=1)	
5	AND	Ra & Rb	Ra & Imm	No	Rc (Ra if INS(8)=1)	"bitwise" logical
6	CMP	Ra - Rb	Ra - Imm	Yes	no	comparison
7	LSR, ASR, XSR, LSL	depends on SHIFTOPC		Yes ²	Ra	shift

&	16 bit C++ bitwise AND operator
---	---------------------------------

¹FlagC

- 1 bit flip-flop in CPU used to store carry for multi-word addition and shifts
- Holds previous value unless written

C = FlagC.Q

²Shift instructions write FlagC with *last bit shifted out*

Figure 9: Simulating EEP1 ALU instruction detailed operation